

 


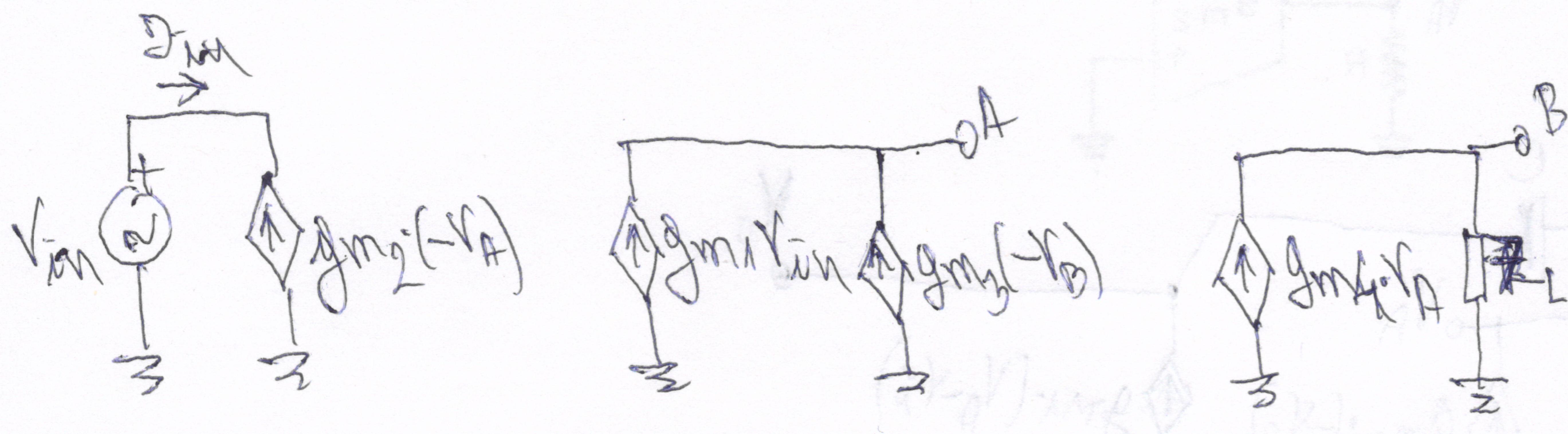- 1) Odrediti prenosnu funkciju kola sa slike i funkciju koje ono obavlja kada je  $g_{m2} \cdot R = 1$ .



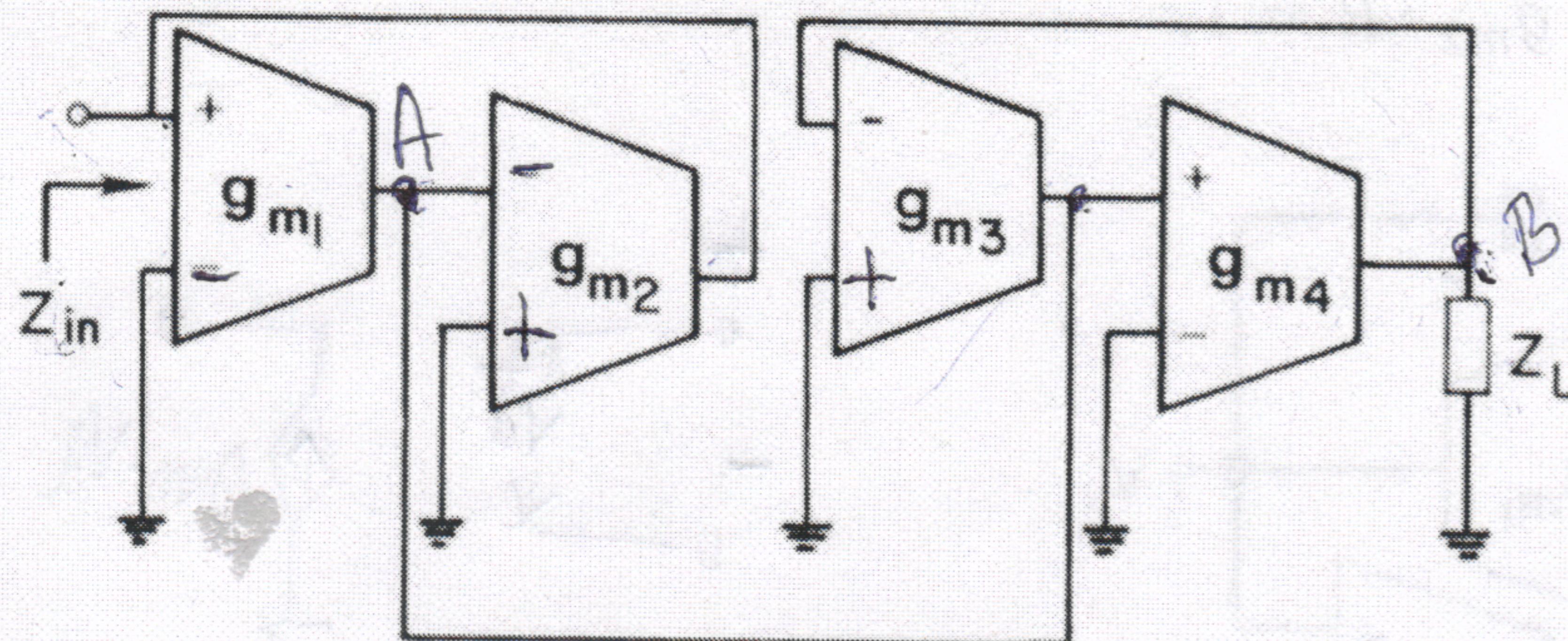2) Odrediti ulaznu impedansu kola sa slike.



$$V_B = Z_L \cdot g_{m4} \cdot V_A$$

$$g_{m1} V_{in} - g_{m3} V_B = 0$$

$$I_{in} = g_{m2} \cdot V_A$$

$$g_{m1} \cdot V_{in} - g_{m3} \cdot g_{m4} Z_L \cdot V_A = 0$$




$$V_A = \frac{V_{in} g_{m1}}{g_{m3} \cdot g_{m4} Z_L}$$

$$I_{in} = g_{m2} \cdot \frac{V_{in} g_{m1}}{g_{m3} \cdot g_{m4} Z_L}$$

$$g_{m3} \cdot g_{m4} Z_L$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{g_{m3} \cdot g_{m4} Z_L}{g_{m1} \cdot g_{m2}}$$

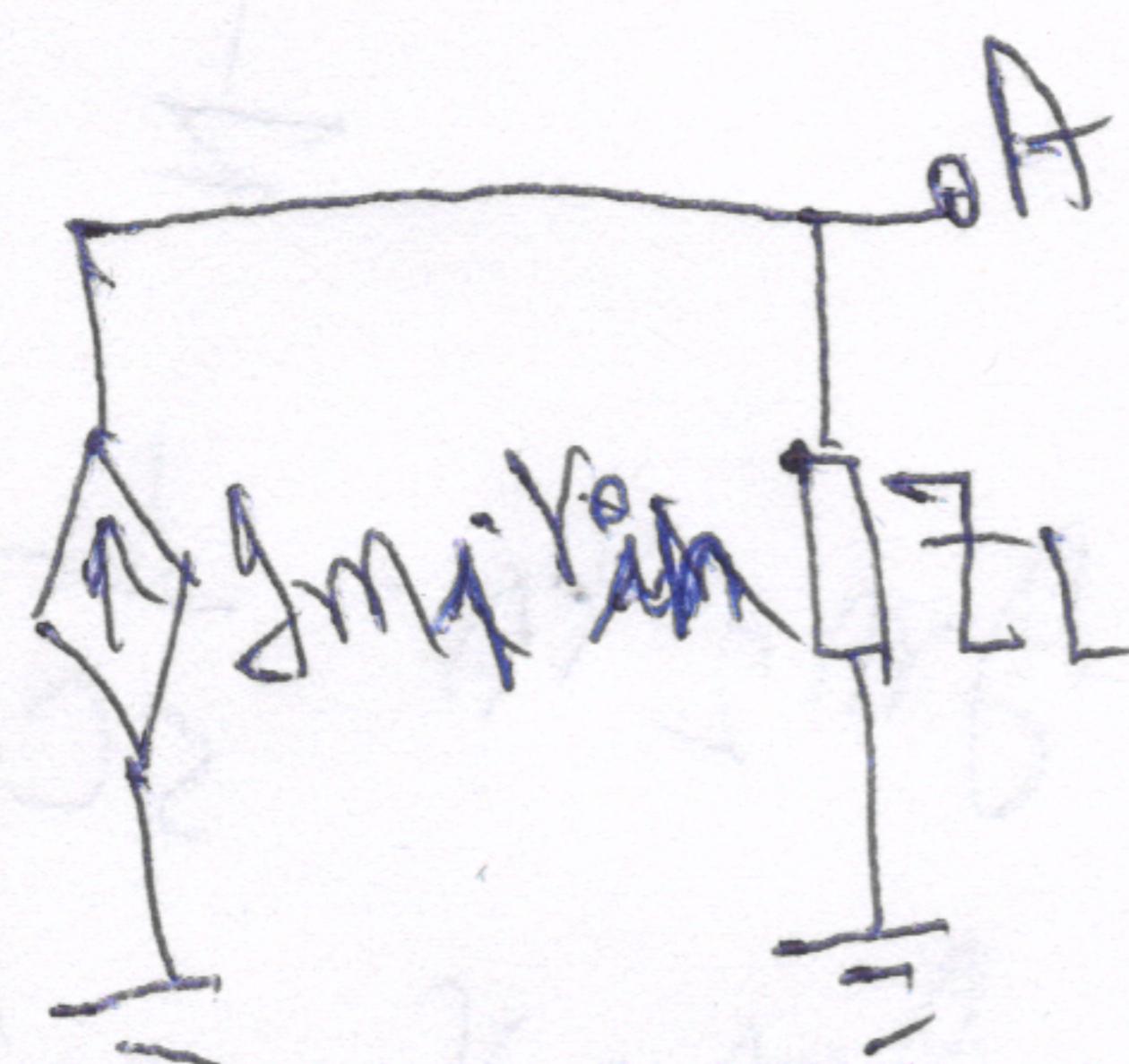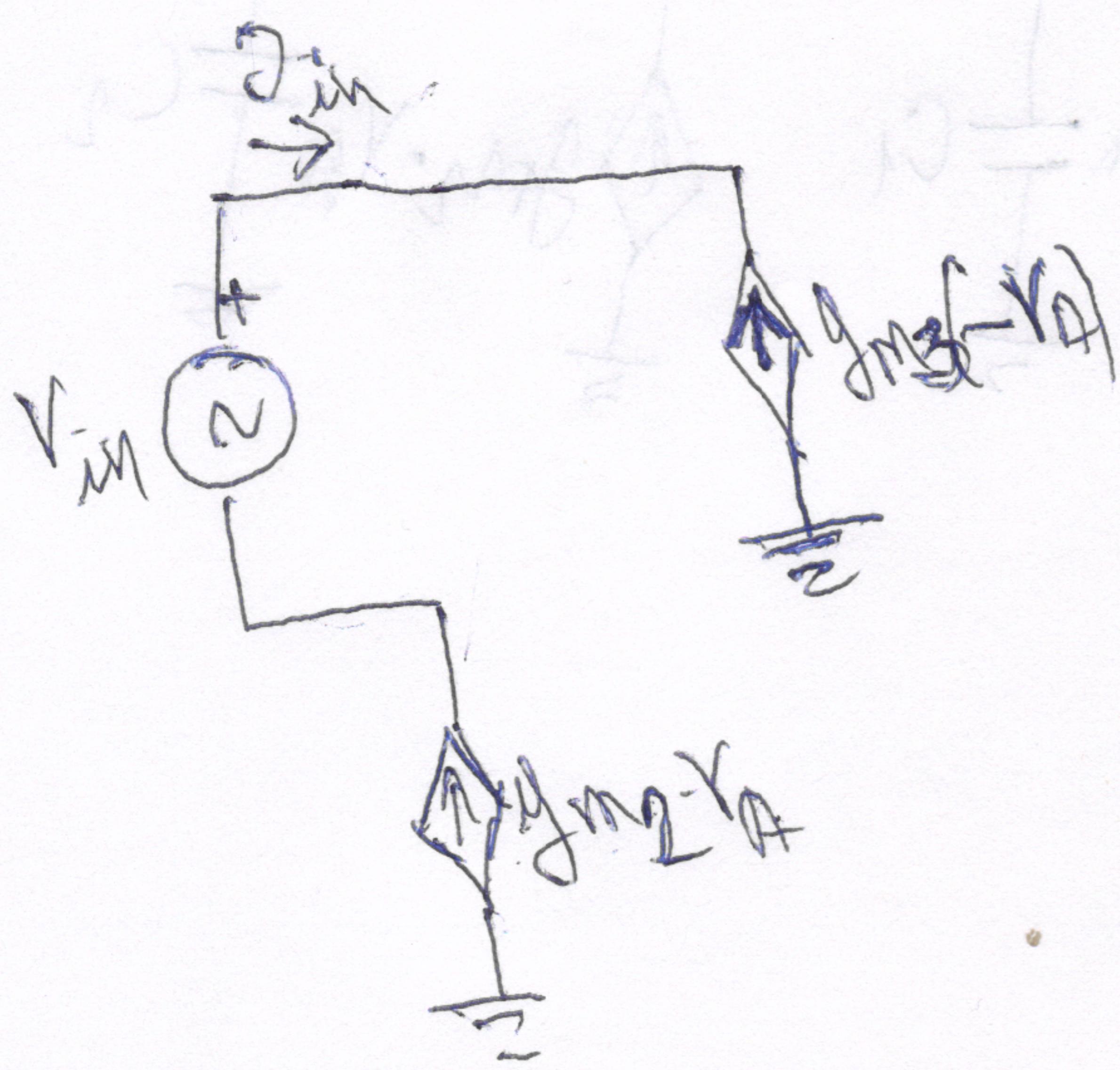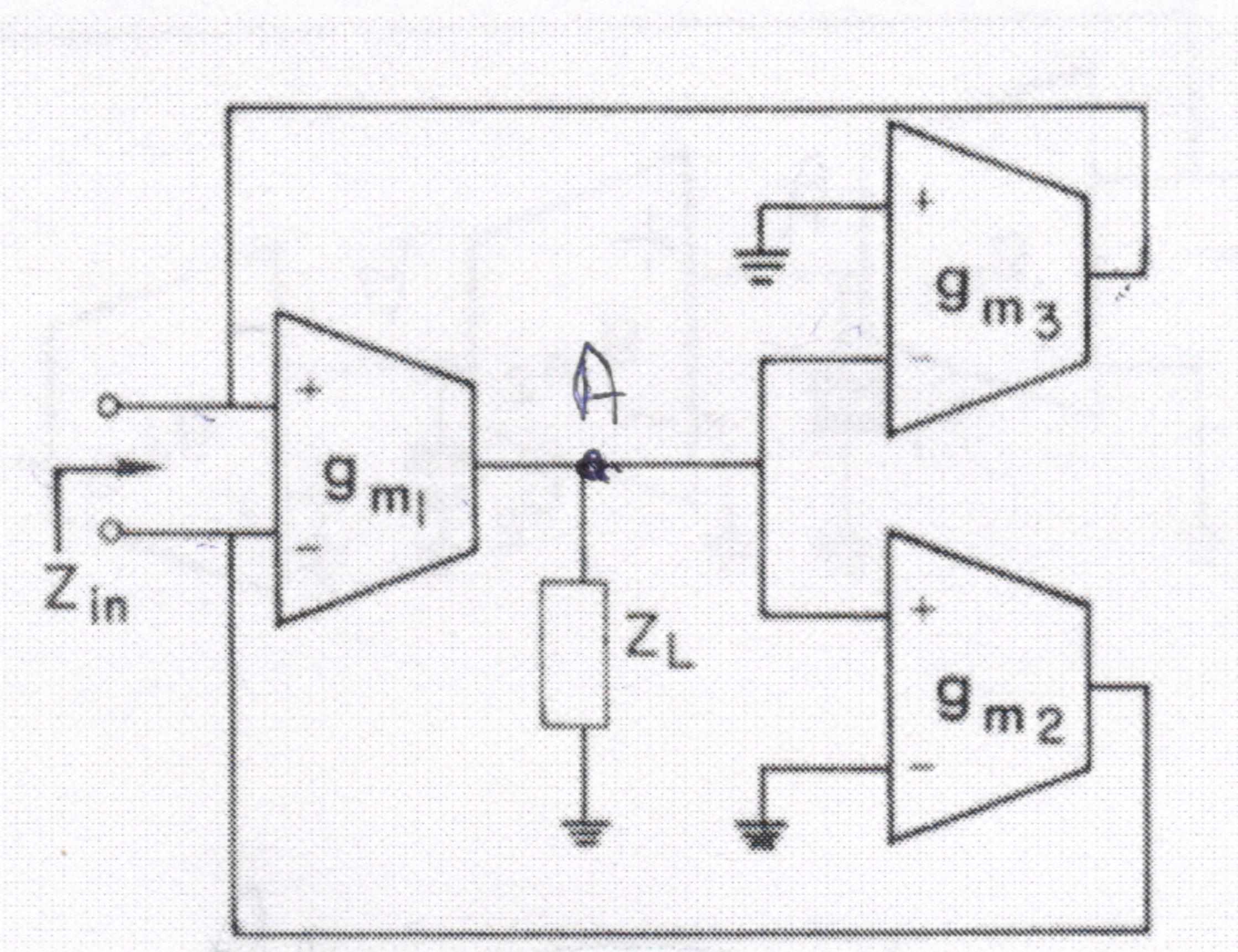3) Na slici je prikazan konvertor impedanse. Odrediti analitički izraz za izlaznu impedansu ukoliko je opterećenje  $Z_L$  kondenzator kapacitivnosti  $C_L$ .



$$g_{m2} = g_{m3}$$

$$V_A = Z_L \cdot g_{m1} \cdot V_{in}$$

$$I_{in} = g_{m2} \cdot V_A$$

$$I_{in} = g_{m2} \cdot g_{m1} \cdot Z_L \cdot V_{in}$$



$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{1}{g_{m1} \cdot g_{m2} \cdot Z_L}$$

$$Z_L = \frac{1}{j\omega C_L}$$

$$Z_{in} = \frac{1}{g_{m1} \cdot g_{m2}} \cdot j\omega C_L$$

$$Z_{in} = \frac{C_L}{g_{m1} \cdot g_{m2}}$$

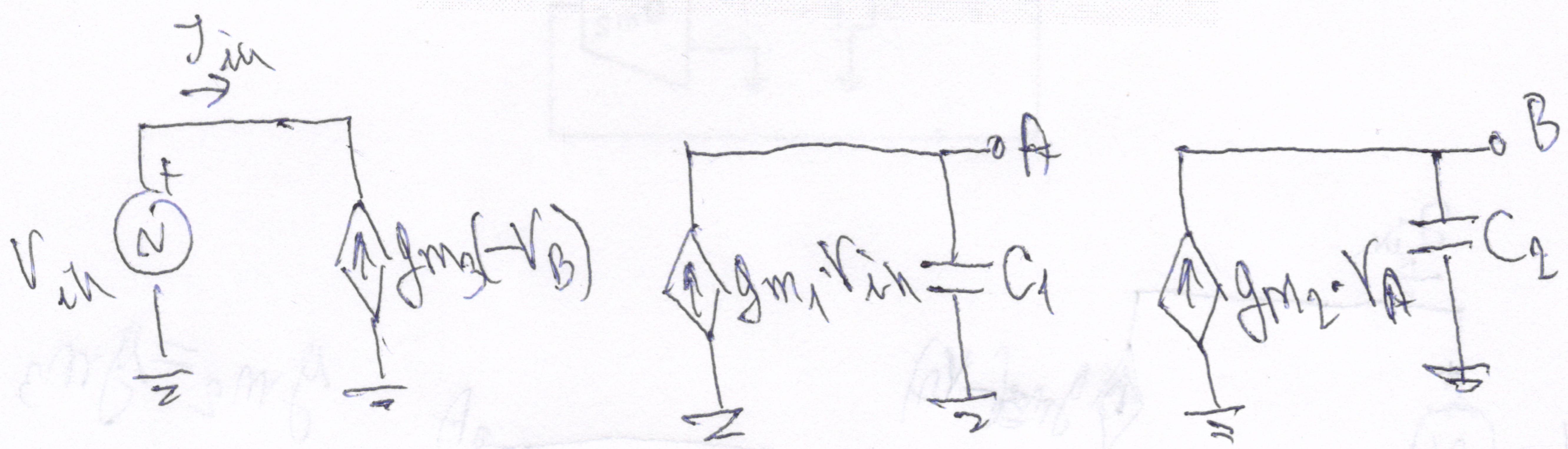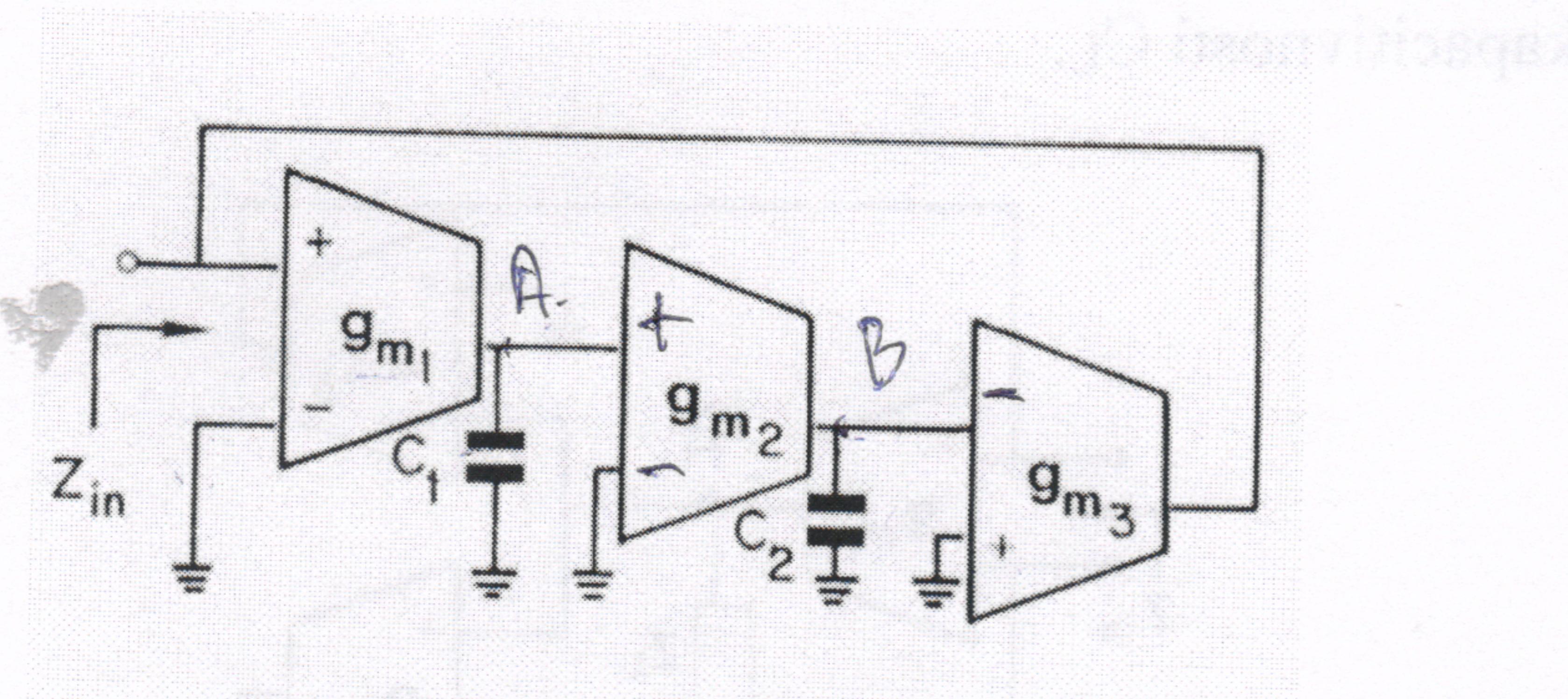4) Dokazati da se kolom sa slike realizuje superinduktivnost  
 $Z = -L \cdot \omega^2$



$$V_B = g_{m2} V_A \cdot \frac{1}{SC_2}$$

$$V_A = g_{m1} V_{in} \cdot \frac{1}{SC_1}$$

$$\underline{I_{in} = g_{m3} V_B}$$

$$V_B = g_{m2} \cdot \frac{1}{SC_2} \cdot g_{m1} \cdot \frac{1}{SC_1} \cdot V_{in}$$

$$I_{in} = g_{m3} g_{m2} g_{m1} \frac{1}{SC_1} \cdot \frac{1}{SC_2} \cdot V_{in}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{1}{SC_1 \cdot SC_2} \cdot \frac{g_{m1} g_{m2} g_{m3}}{g_{m1} g_{m2} g_{m3}}$$

$$Z_{in} = -L \cdot \omega^2$$

$$L = \frac{C_1 C_2}{g_{m1} g_{m2} g_{m3}}$$