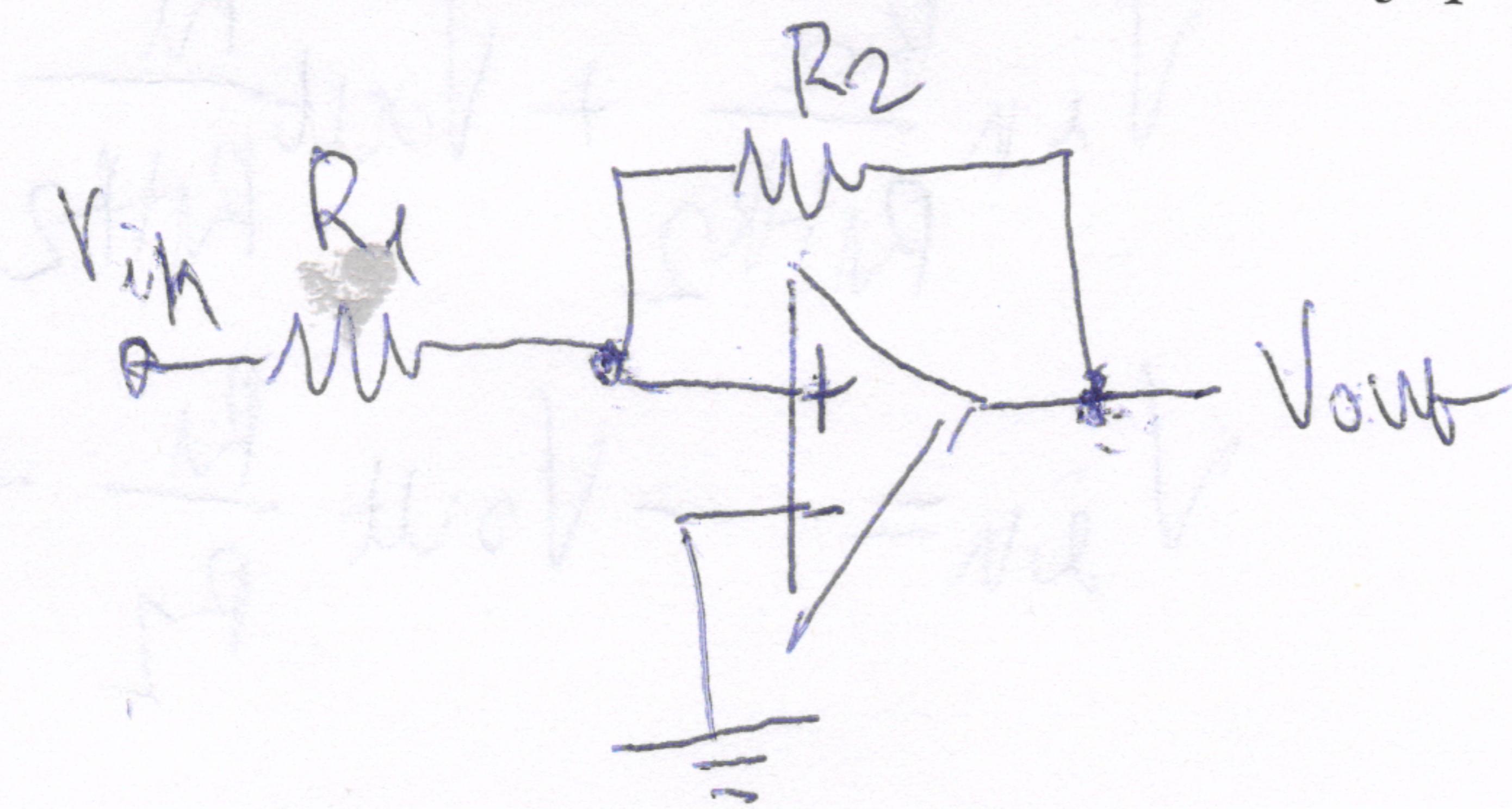


1) Naponski novo logičke jedinice je $V_{OH}=2$ V, a logičke nule $V_{OL}=-2$ V.

Odrediti elemente neinvertujućeg Šmitovog komparatora tako da:

- gornji prag okidanja bude 1 V, donji prag okidanja 0 V.
- gornji prag okidanja bude 0 V, a donji prag okidanja -1V.



$$V^+ = \frac{R_2}{R_1 + R_2} \cdot V_{in} + \frac{R_1}{R_1 + R_2} \cdot V_{out}$$


$$V_{out} = V_{OL}$$

$$\frac{R_2}{R_1 + R_2} \cdot V_{in} + \frac{R_1}{R_1 + R_2} \cdot V_{OL} = 0$$

$$V_{in} = -\frac{R_1}{R_2} \cdot V_{OL}$$

$$V_{ut} = -\frac{R_1}{R_2} \cdot V_{OH}$$


$$V_{out} = V_{OH}$$

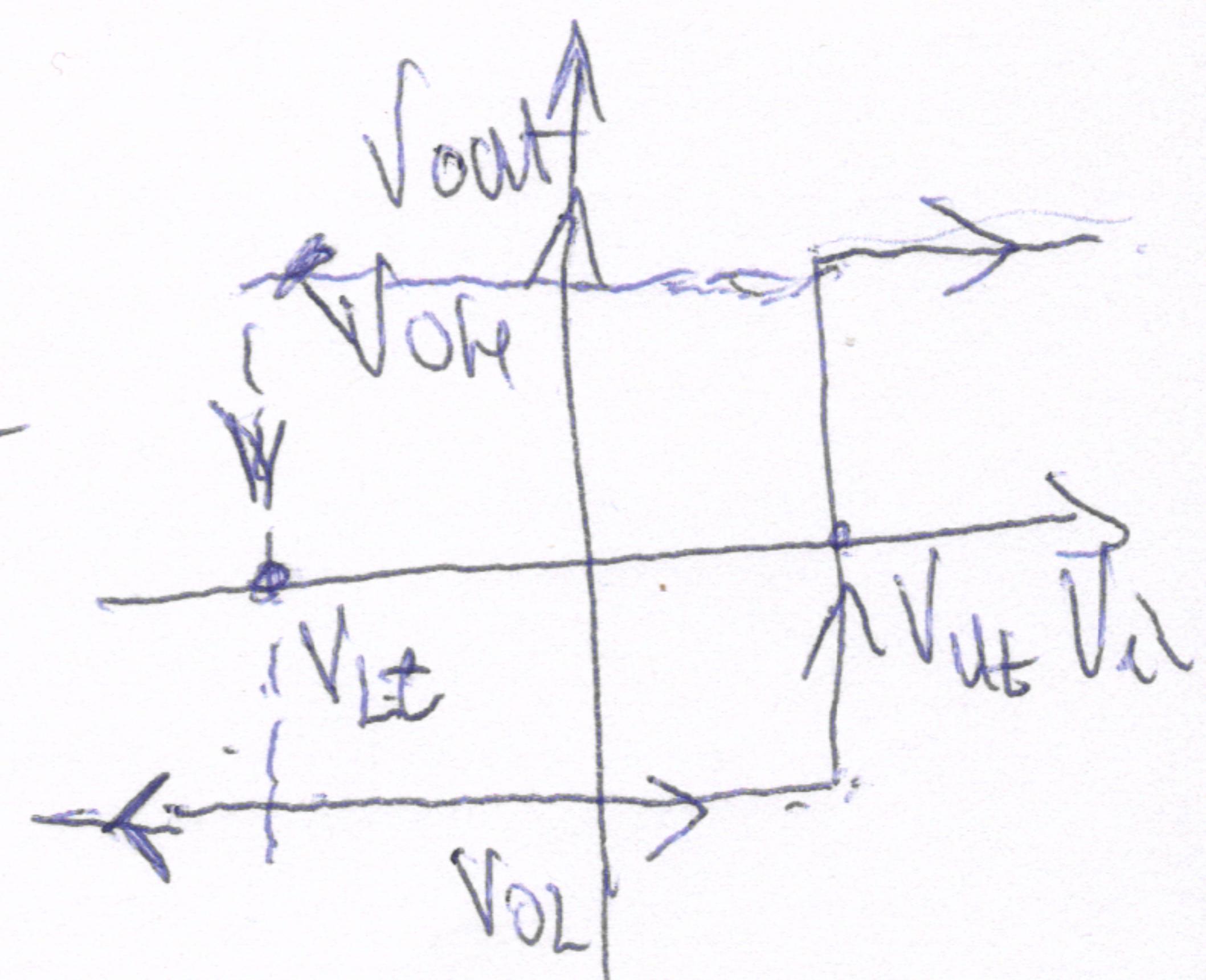

$$\frac{R_2}{R_1 + R_2} \cdot V_{in} + \frac{R_1}{R_1 + R_2} \cdot V_{OH} = 0$$

$$V_{in} = -\frac{R_1}{R_2} \cdot V_{OH}$$
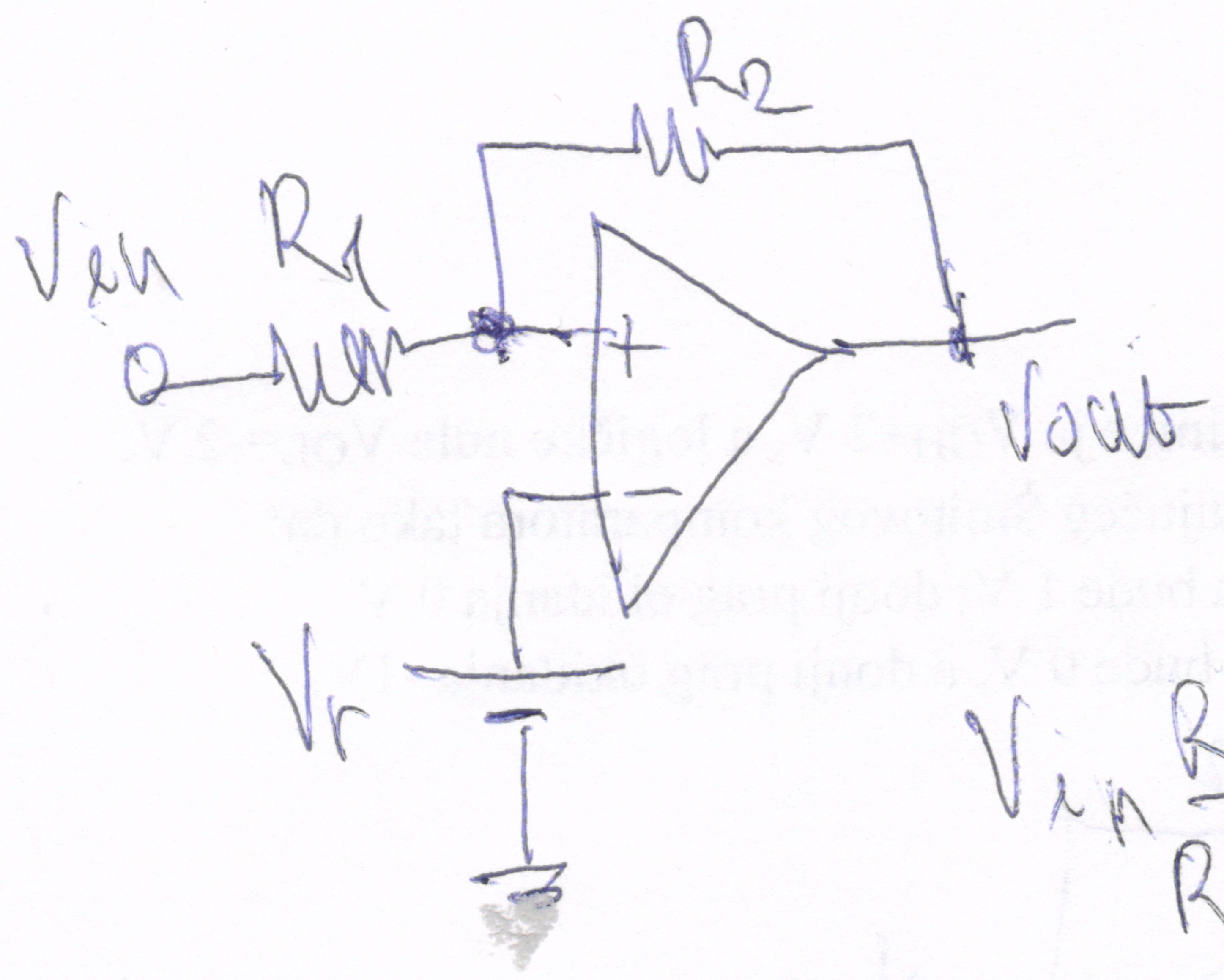
$$V_{ut} = -\frac{R_1}{R_2} \cdot V_{OH}$$



$$V_{in} \frac{R_2}{R_1 + R_2} + V_{out} \frac{R_1}{R_1 + R_2} = V_r$$

$$V_{in} = -V_{out} \cdot \frac{R_1}{R_2} + \left(\frac{R_1 + R_2}{R_2} \right) V_r$$

$$V_{out} = V_{OL}$$

$$V_{at} = -V_{OL} \frac{R_1}{R_2} + \left(1 + \frac{R_1}{R_2} \right) V_r$$

$$V_{out} = V_{OH}$$

$$V_{at} = -V_{OH} \frac{R_1}{R_2} + \left(1 + \frac{R_1}{R_2} \right) V_r$$

$$V_{at} = 1V \quad V_{LT} = 0V$$

$$V_{at} - V_{LT} = V_{OH} \frac{R_1}{R_2} - V_{OL} \frac{R_1}{R_2} = 1V$$

$$V_{at} - V_{LT} = (V_{OH} - V_{OL}) \frac{R_1}{R_2} = 1$$

$$\frac{R_1}{R_2} = \frac{1}{4}$$

$$V_r \left(1 + \frac{R_1}{R_2} \right) - V_{OH} \frac{R_1}{R_2} = 0$$

$$V_r = 0,5V \cdot \frac{4}{5} = 0,4V$$

$$V_r = 0,4V$$


2) Dominantni pol komparatora je na frekvenciji $\omega_p = 10^3$ rad/s,

jednosmerno pojačanje komparatora je $A_0 = 10^4$ a slurejt $1V/\mu s$. Ukoliko se naponski nivo logičke jedinice i logičke nule razlikuju za $1 V$, odrediti vreme odziva komparatora na signal čija je amplituda

- a) $V_{in} = 10 \text{ mV}$
- b) $V_{in} = 0,2 \text{ V}$

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_p}} = \frac{A_0}{1 + s \cdot T_p}$$

$$V_{out}(s) = A(s) \cdot V_{in}(s)$$

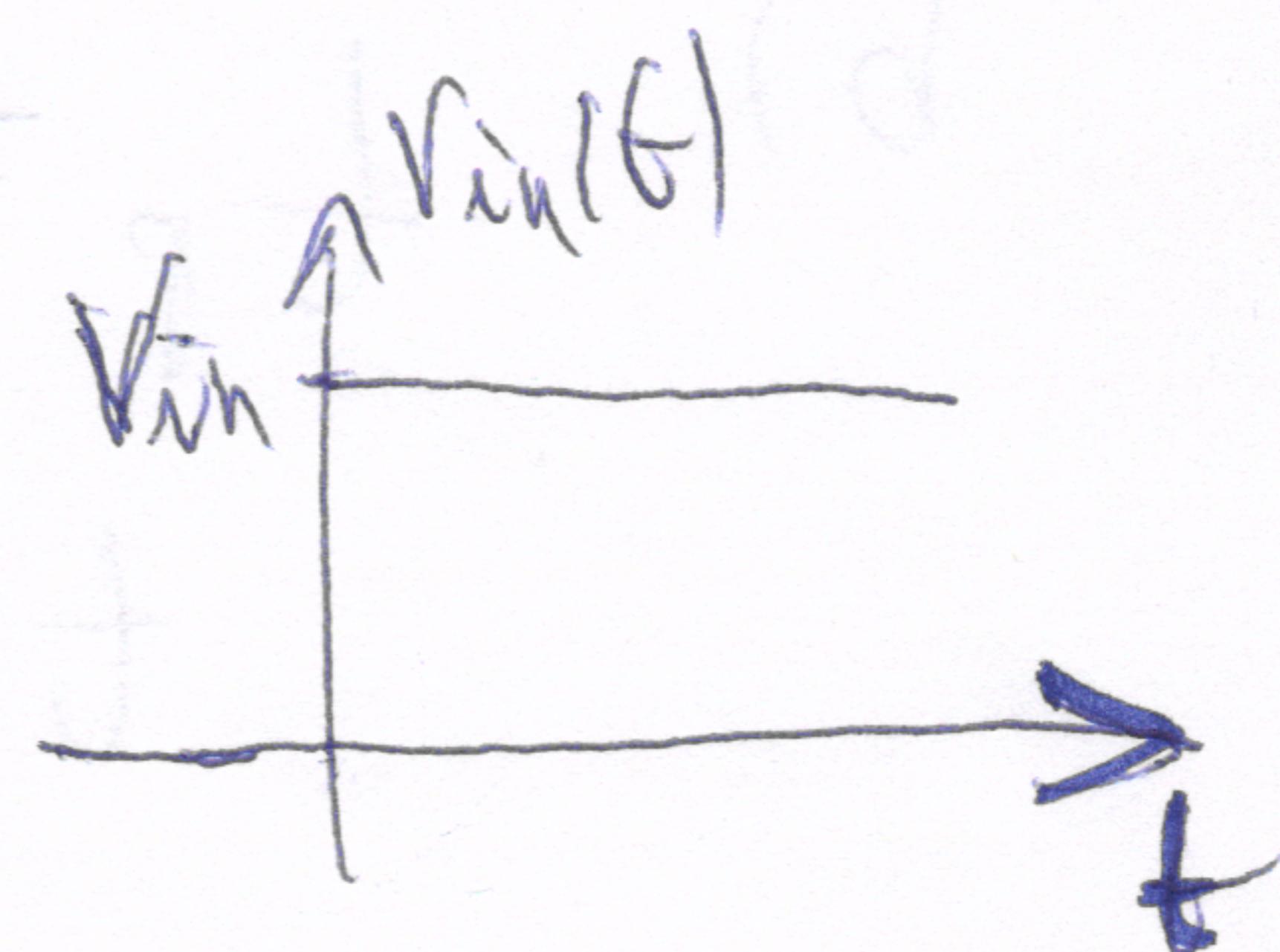


$$V_{in}(s) = \frac{V_{in}}{s}$$

$$V_{out}(s) = \frac{A_0}{1 + s T_p} \cdot \frac{1}{s}$$

$$V_{out}(t) = L^{-1} \left\{ \frac{A_0}{1 + s T_p} - \frac{1}{s} \right\}$$
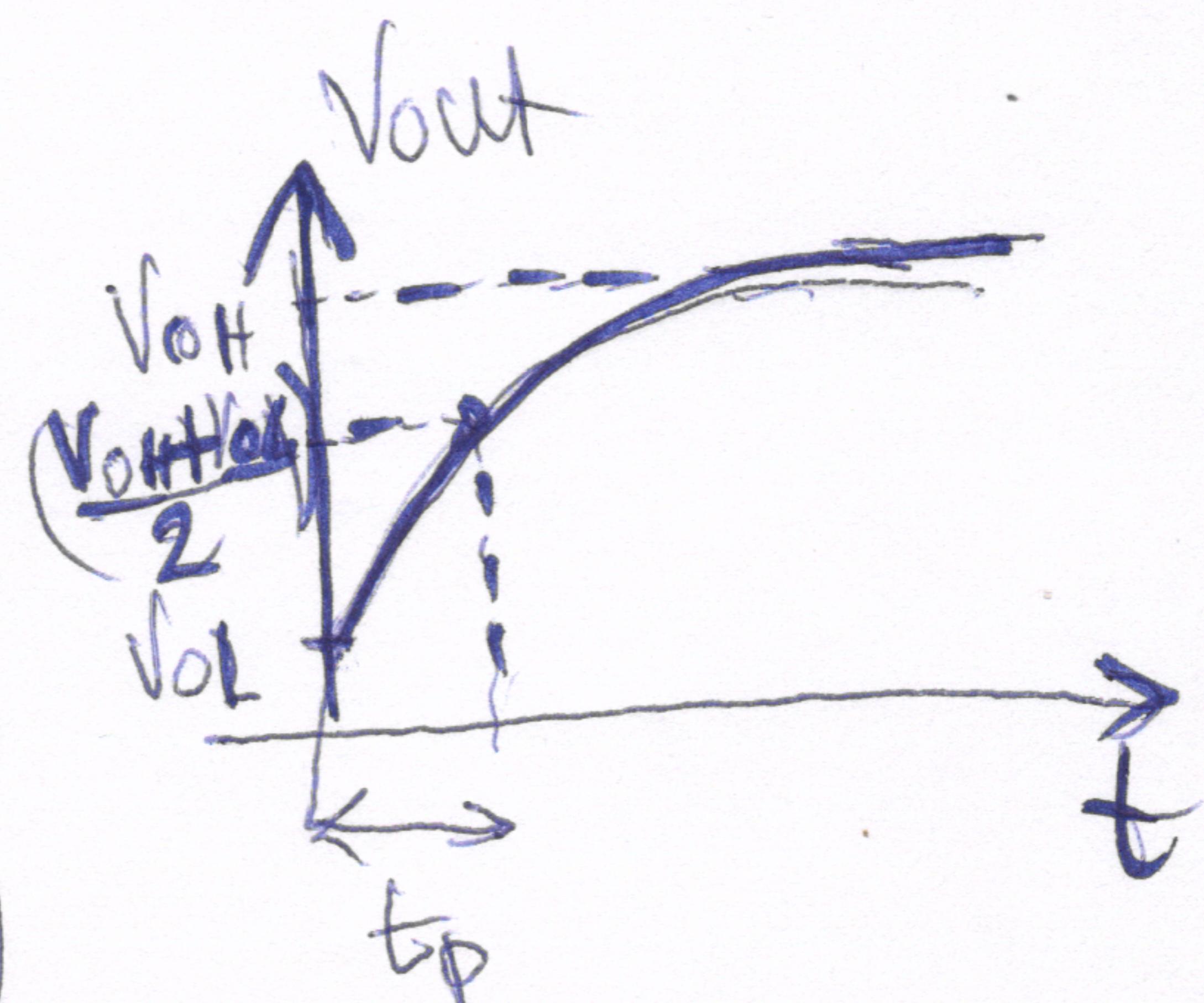
$$V_{out} = A_0 \cdot V_{in} \left(1 - e^{-\frac{t}{T_p}} \right)$$



$$A_0 \cdot V_{in} \left(1 - e^{-\frac{t_p}{T_p}} \right) = \frac{V_{H+L}}{2}$$

$$e^{-\frac{t_p}{T_p}} = \left(1 - \frac{V_{H+L}}{2 A_0 \cdot V_{in}} \right)$$

$$t_p = T_p \cdot \ln \frac{2 A_0 V_{in}}{2 A_0 V_{in} - (V_{H+L})} = 10^{-3} \ln \frac{2 \cdot 10^4 \cdot 10^3}{2 \cdot 10^2 - 1}$$


$$t_p = 5,01 \text{ ms}$$

$$t_{P\min} = \frac{V_{OH} - V_{OL}}{2 \cdot SR} = \frac{1}{2 \cdot 10^6} = 0,5 \cdot 10^{-6} \text{ s}$$

$$t_{P\min} = 0,5 \text{ MS}$$

b) $t_p = 2,5 \cdot 10^{-9} = 0,25 \text{ MS}$

$$t_p < t_{P\min}$$

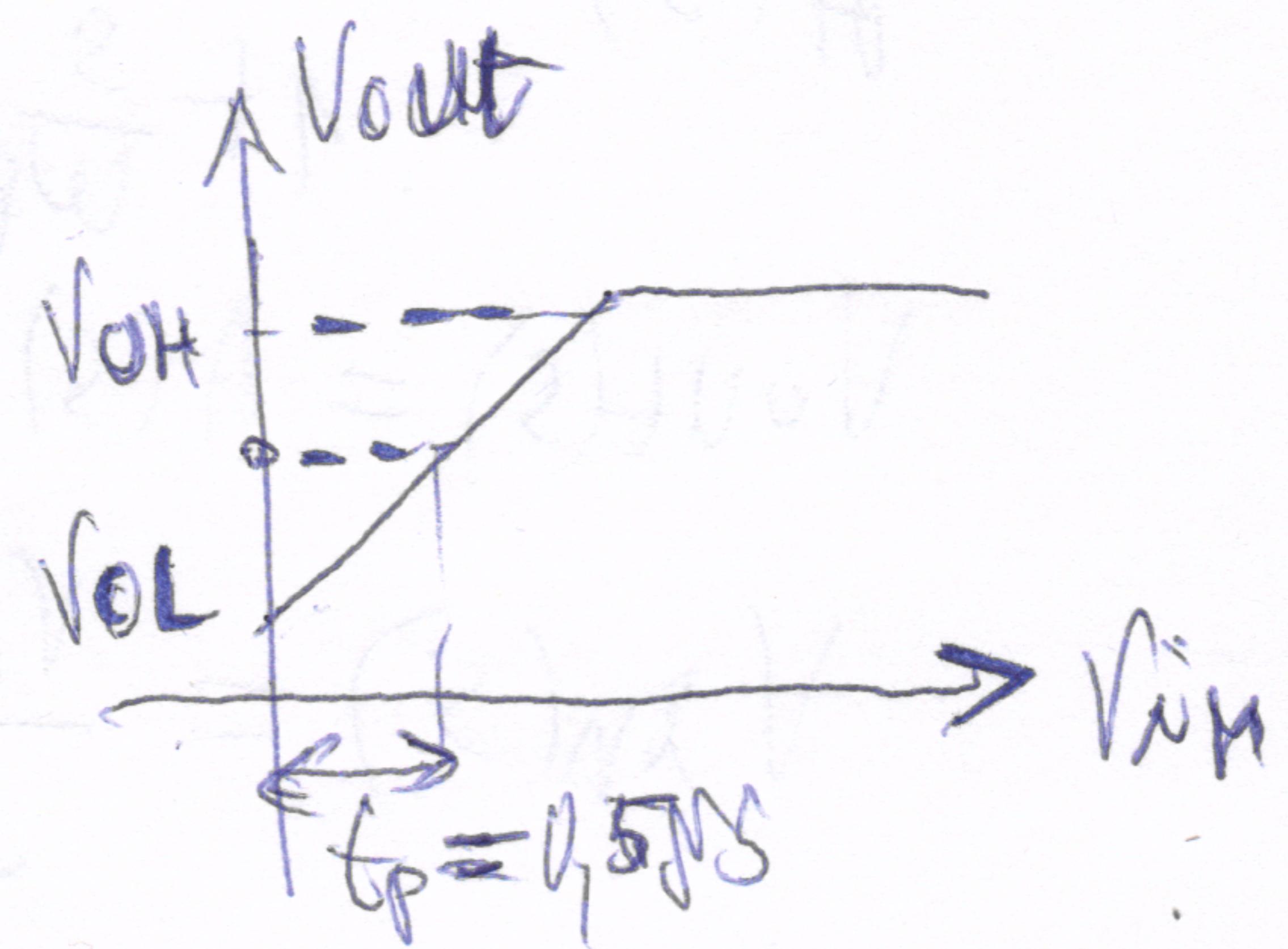

$$t_p = t_{P\min} = 0,5 \text{ MS}$$