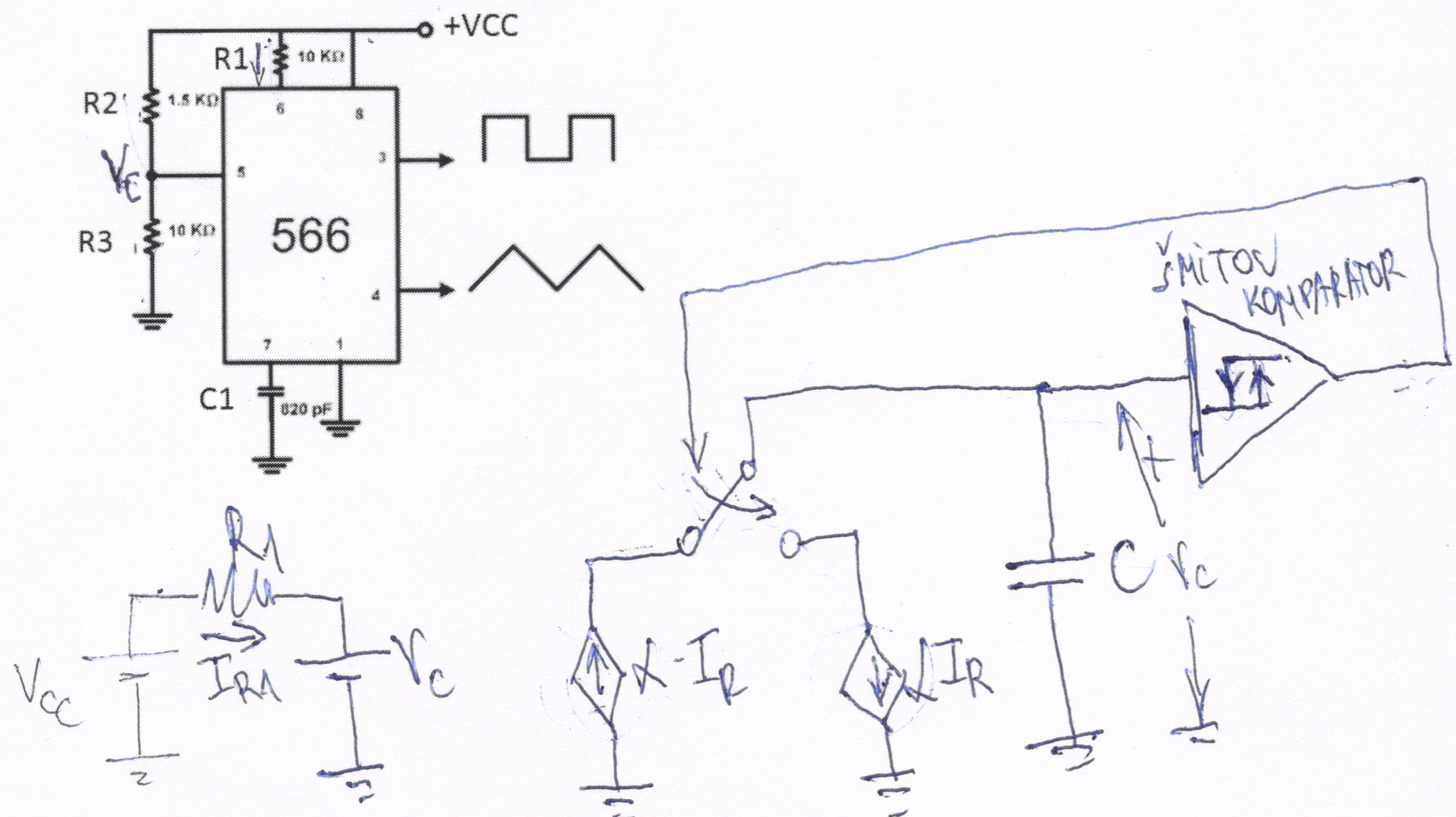


1. Za kolo naponom kontrolisanog oscilatora, prikazano na slici odrediti kontrolni napon i frekvenciju slobodnog oscilovanja, fo. Histerezis Šmitovog komparatora iznosi 3 V. Poznato je:  $R_1 = 10\text{k}\Omega$ ;  $R_2 = 1.5\text{k}\Omega$ ;  $R_3 = 10\text{k}\Omega$ ;  $C = 820\text{ pF}$ ;  $V_{CC} = 12\text{ V}$ .



$$V_c(t_1) = V_L - \frac{1}{R_1 C} \int_{t_1}^{t_2} I_R(t) dt + V_C$$

NOTAKO HYZA; GORE UPUT OKUGAHTA

$$V_c(t_1 + \Delta t) = \frac{1}{C} \int_0^{\Delta t} I_R(t) dt + V_C$$

$$I_R(t) = \frac{V_{CC} - V_c}{R_1}$$

$$V_c(t_1 + \Delta t) = \frac{1}{C} \frac{(V_{CC} - V_c)}{R_1} \cdot \Delta t + V_C$$

$$V_c(t_1 + \frac{T}{2}) = \frac{1}{C} \cdot \frac{(V_{CC} - V_c)}{R_1} \cdot \frac{T}{2} + V_C = V_{TH}$$

$$T = \frac{2(V_{TH} - V_C)}{(V_{CC} - V_C)} \cdot C \cdot R_1$$


$$H = V_{TH} - V_{TL} = 3V$$

$$V_{CC} - V_C = V_{CC} - \frac{R_3}{R_2 + R_3} \cdot V_{CC} = \left(1 - \frac{10}{11,5}\right) \cdot 12$$

$$f_0 = \frac{1}{T} = \frac{(V_{CC} - V_C)}{2(V_{TH} - V_{TL}) C R_L} = 32,5 \text{ kHz}$$

$$f_0 = \frac{2}{R_L C} \frac{\underline{V_{CC} - V_C}}{\underline{V_{CC}}}$$

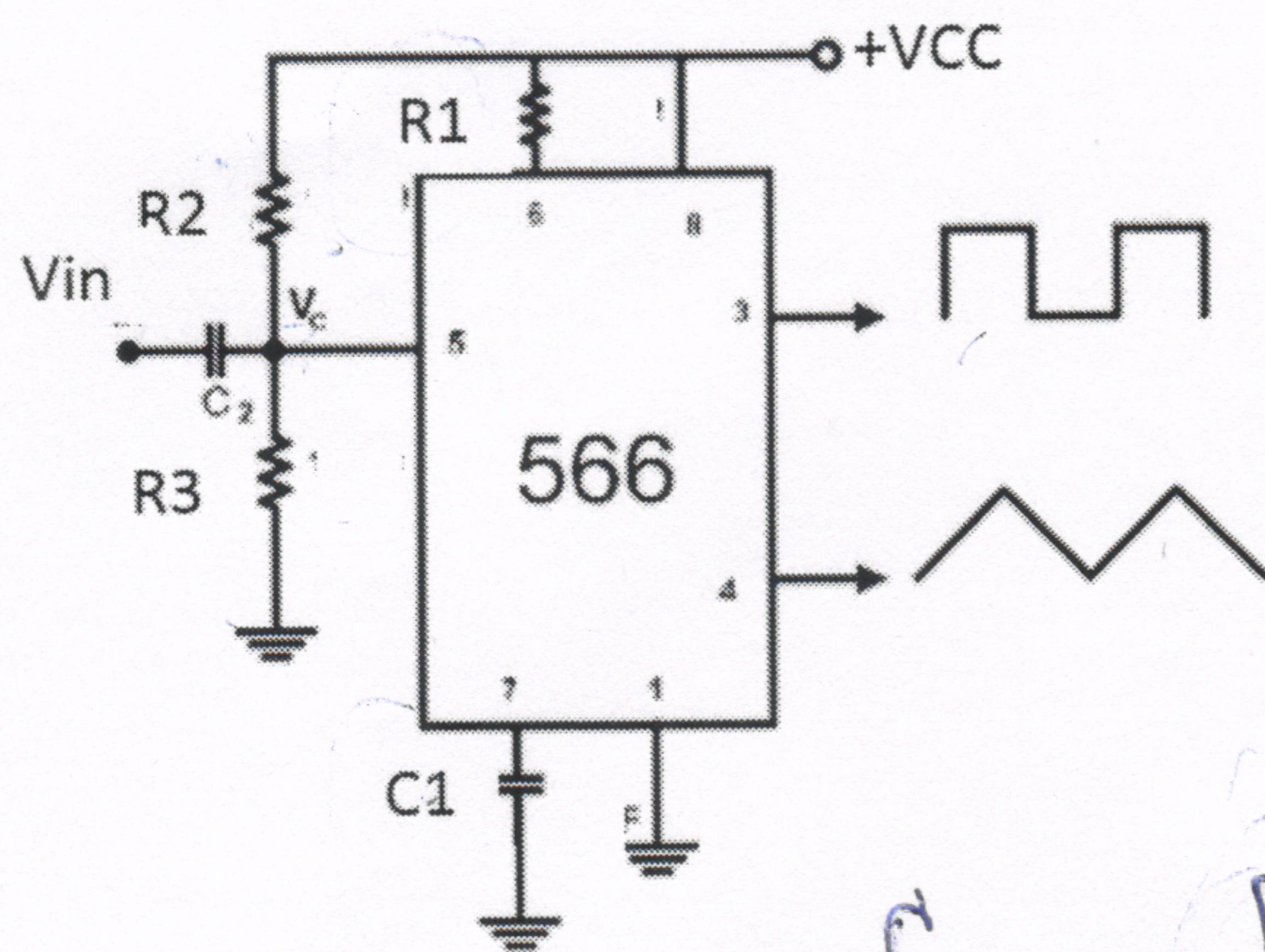2. Za kolo naponom kontrolisanog oscilatora, prikazano na slici odrediti elemente kola tako da frekvencija slobodnog oscilovanja iznosi  $f_0 = 30 \text{ kHz}$ , a osetljivost naponom kontrolisanog oscilatora  $K_{VCO} = 15000 \frac{\text{Hz}}{\text{V}}$ . Histerezis Šmitovog komparatora iznosi 3 V. Poznato je  $V_{CC} = 12 \text{ V}$ .



$$f_{\text{tot}} = f_0 + K_{VCO} \cdot V_{\text{in}}$$

$$f_c(t) = V_c + V_{\text{cm}} \sin \omega t$$

$$f_{\text{tot}} = \frac{[V_{CC} - V_c - V_{\text{cm}} \sin \omega t]}{2(V_{TH} - V_{TL})} \cdot \frac{1}{C_1 R_1}$$

$$f_0 = \frac{(V_{CC} - V_c)}{2(V_{TH} - V_{TL})} \cdot \frac{1}{C_1 R_1}$$

$$R_1 = 12,5 \text{ k}\Omega$$

$$C_1 = 1 \text{ nF}$$

$$C_1 R_1 = 1,25 \cdot 10^{-5} \text{ s}$$

$$K_{VCO} = \frac{1}{2(V_{TH} - V_{TL}) \cdot C_1 R_1}$$

$$C_1 R_1 = \frac{1}{2(V_{TH} - V_{TL}) \cdot K_{VCO}}$$

$$T_F = C_1 R_1 = \frac{1}{6V \cdot (15000 \frac{\text{Hz}}{\text{V}})} = 1,25 \cdot 10^{-5} \text{ s}$$

$$f_0 = \frac{(V_{cc} - V_c)}{2(V_{thH} - V_{thL})} \cdot \frac{1}{CR_L} = (V_{cc} - V_c) \cdot K_{vco}$$

$$V_{cc} - V_c = \frac{f_0}{K_{vco}}$$

$$V_c = V_{cc} = \frac{f_0}{K_{vco}} = 12V - \frac{3 \cdot 10^4 \text{ Hz}}{1.5 \cdot 10^4 \text{ Hz}}$$

$$V_c = 12V - 2V = 10V$$

$$V_c = \frac{R_3}{R_2 + R_3} \cdot V_{cc}$$

$$1 + \frac{R_2}{R_3} = \frac{V_{cc}}{V_c} = A_f$$

$$\boxed{\frac{R_2}{R_3} = 0.2}$$

$$\begin{aligned} R_2 &= 2k\Omega \\ R_3 &= 10k\Omega \end{aligned}$$